

Introduction to Electrical Circuits

Final Term Lecture - 04

Reference Book:

Introductory Circuit Analysis

Robert L. Boylestad, 11th Edition



Series Parallel Network Analysis

- In general, when working with series-parallel ac networks, consider the following approach:
 - *Redraw the network, using block impedances to combine obvious series and parallel elements, which will reduce the network to one that clearly reveals the fundamental structure of the system.*
 - *Study the problem and make a brief mental sketch of the overall approach you plan to use. Doing this may result in time- and energy-saving shortcuts.*
 - *After the overall approach has been determined, it is usually best to consider each branch involved in your method independently before tying them together in series-parallel combinations.*
 - *When you have arrived at a solution, check to see that it is reasonable by considering the magnitudes of the energy source and the elements in the circuit.*



Example: For the network in following Fig. 16.1:

- Calculate \mathbf{Z}_T .
- Determine \mathbf{I}_s .
- Calculate \mathbf{V}_R and \mathbf{V}_C .
- Find \mathbf{I}_C .
- Compute the power delivered.
- Find F_p of the network.

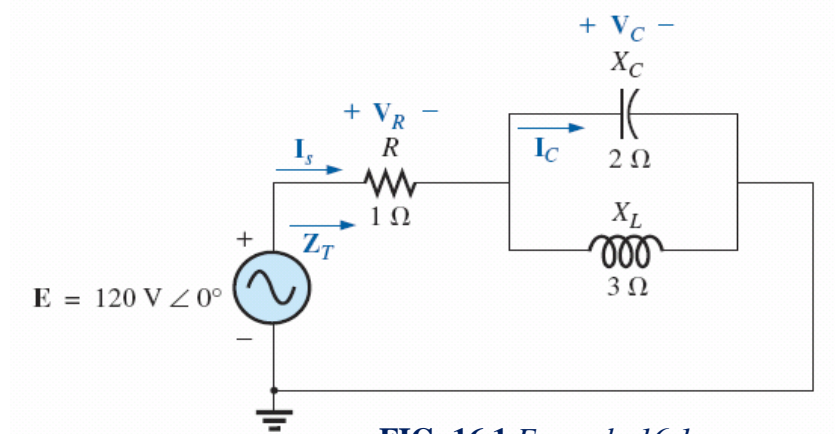


FIG. 16.1 Example 16.1.

Solutions:

The total impedance is defined by

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2$$

$$\mathbf{Z}_1 = R \angle 0^\circ = 1 \Omega \angle 0^\circ$$

$$\begin{aligned} \mathbf{Z}_2 = \mathbf{Z}_C \parallel \mathbf{Z}_L &= \frac{(X_C \angle -90^\circ)(X_L \angle 90^\circ)}{-jX_C + jX_L} = \frac{(2 \Omega \angle -90^\circ)(3 \Omega \angle 90^\circ)}{-j2 \Omega + j3 \Omega} \\ &= \frac{6 \Omega \angle 0^\circ}{j1} = \frac{6 \Omega \angle 0^\circ}{1 \angle 90^\circ} = 6 \Omega \angle -90^\circ \end{aligned}$$

and

$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 1 \Omega - j6 \Omega = 6.08 \Omega \angle -80.54^\circ$$

$$\text{b. } \mathbf{I}_s = \frac{\mathbf{E}}{\mathbf{Z}_T} = \frac{120 \text{ V} \angle 0^\circ}{6.08 \Omega \angle -80.54^\circ} = 19.74 \text{ A} \angle 80.54^\circ$$

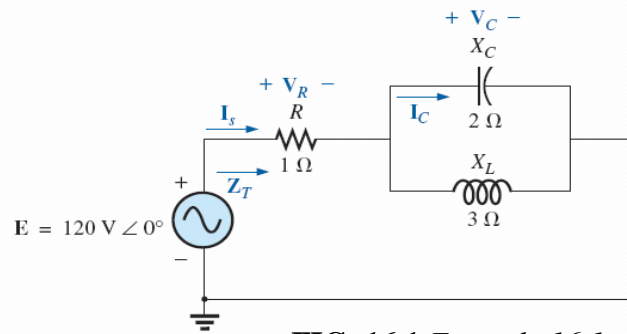


FIG. 16.1 Example 16.1.

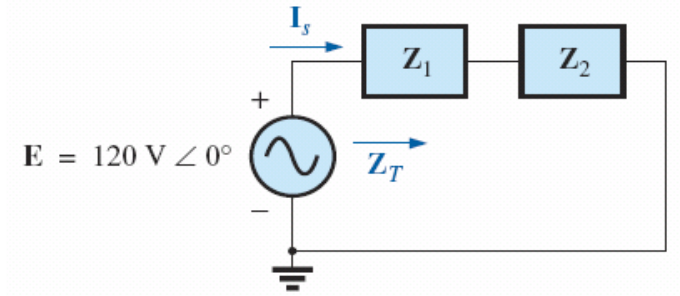


FIG. 16.2 Network in Fig. 16.1 after assigning the block impedances.

- c. Referring to Fig. 16.2, we find that V_R and V_C can be found by a direct application of Ohm's law:

$$V_R = I_s Z_1 = (19.74 \text{ A } \angle 80.54^\circ)(1 \Omega \angle 0^\circ) = \mathbf{19.74 \text{ V } \angle 80.54^\circ}$$

$$\begin{aligned} V_C &= I_s Z_2 = (19.74 \text{ A } \angle 80.54^\circ)(6 \Omega \angle -90^\circ) \\ &= \mathbf{118.44 \text{ V } \angle -9.46^\circ} \end{aligned}$$

- d. Now that V_C is known, the current I_C can also be found using Ohm's law.

$$I_C = \frac{V_C}{Z_C} = \frac{118.44 \text{ V } \angle -9.46^\circ}{2 \Omega \angle -90^\circ} = \mathbf{59.22 \text{ A } \angle 80.54^\circ}$$

e. $P_{\text{del}} = I_s^2 R = (19.74 \text{ A})^2(1 \Omega) = \mathbf{389.67 \text{ W}}$

f. $F_p = \cos \theta = \cos 80.54^\circ = \mathbf{0.164 \text{ leading}}$



Example: For the network in following Fig. 16.5:

- Calculate the voltage V_C using the voltage divider rule.
- Calculate the current I_s .

Solutions:

- The network is redrawn as shown in Fig. 16.6, with

$$Z_1 = 5 \Omega = 5 \Omega \angle 0^\circ$$

$$Z_2 = -j 12 \Omega = 12 \Omega \angle -90^\circ$$

$$Z_3 = +j 8 \Omega = 8 \Omega \angle 90^\circ$$

$$V_C = \frac{Z_2 E}{Z_1 + Z_2} = \frac{(12 \Omega \angle -90^\circ)(20 \text{ V} \angle 20^\circ)}{5 \Omega - j 12 \Omega} = \frac{240 \text{ V} \angle -70^\circ}{13 \angle -67.38^\circ} = 18.46 \text{ V} \angle -2.62^\circ$$

$$\text{b. } I_1 = \frac{E}{Z_3} = \frac{20 \text{ V} \angle 20^\circ}{8 \Omega \angle 90^\circ} = 2.5 \text{ A} \angle -70^\circ$$

$$I_2 = \frac{E}{Z_1 + Z_2} = \frac{20 \text{ V} \angle 20^\circ}{13 \Omega \angle -67.38^\circ} = 1.54 \text{ A} \angle 87.38^\circ$$

and

$$\begin{aligned} I_s &= I_1 + I_2 \\ &= 2.5 \text{ A} \angle -70^\circ + 1.54 \text{ A} \angle 87.38^\circ \\ &= (0.86 - j 2.35) + (0.07 + j 1.54) \\ I_s &= 0.93 - j 0.81 = 1.23 \text{ A} \angle -41.05^\circ \end{aligned}$$

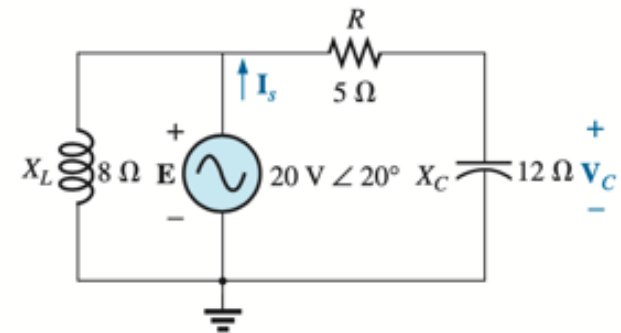


FIG. 16.5

Example 16.3.

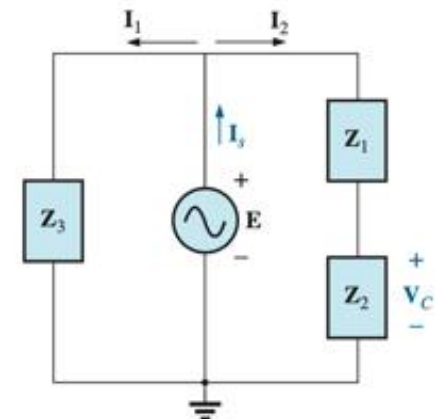


FIG. 16.6


Network in Fig. 16.5 after assigning the block impedances.

Example: For the network in following Figure:

- Compute \mathbf{I} .
- Find \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 .
- Verify Kirchhoff's current law by showing that

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$$

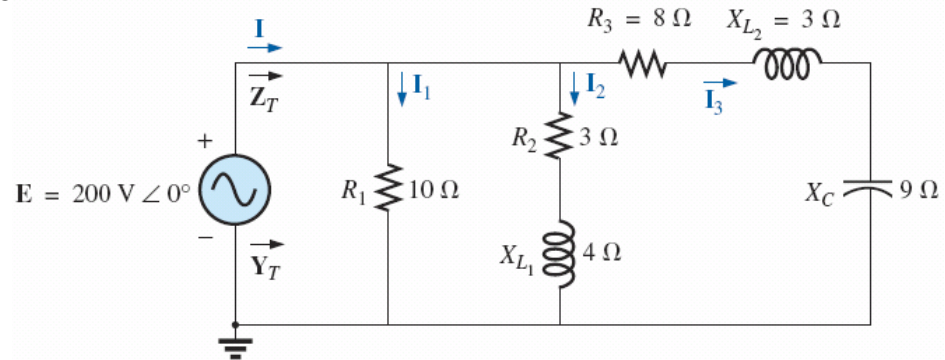- Find the total impedance of the circuit.



Solutions:

- Redrawing the circuit as in Fig. 17.15 reveals a strictly parallel network where


$$\mathbf{Z}_1 = R_1 = 10 \Omega \angle 0^\circ$$

$$\mathbf{Z}_2 = R_2 + jX_{L1} = 3 \Omega + j4 \Omega$$

$$\mathbf{Z}_3 = R_3 + jX_{L2} - jX_C = 8 \Omega + j3 \Omega - j9 \Omega = 8 \Omega - j6 \Omega$$

The total admittance is

$$\begin{aligned} \mathbf{Y}_T &= \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3 \\ &= \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} = \frac{1}{10 \Omega} + \frac{1}{3 \Omega + j4 \Omega} + \frac{1}{8 \Omega - j6 \Omega} \\ &= 0.1 \text{ S} + \frac{1}{5 \Omega \angle 53.13^\circ} + \frac{1}{10 \Omega \angle -36.87^\circ} \\ &= 0.1 \text{ S} + 0.2 \text{ S} \angle -53.13^\circ + 0.1 \text{ S} \angle 36.87^\circ \\ &= 0.1 \text{ S} + 0.12 \text{ S} - j0.16 \text{ S} + 0.08 \text{ S} + j0.06 \text{ S} \\ &= 0.3 \text{ S} - j0.1 \text{ S} = 0.316 \text{ S} \angle -18.435^\circ \end{aligned}$$

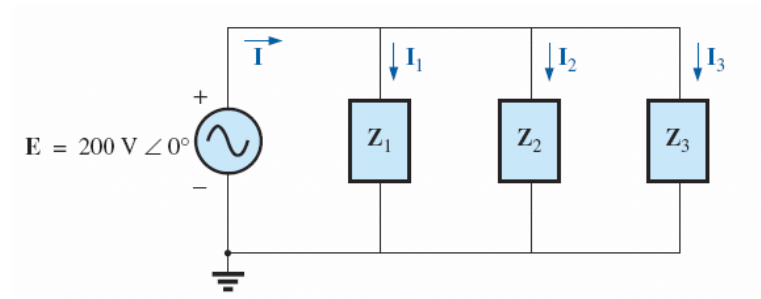

The current \mathbf{I} is given by

$$\begin{aligned} \mathbf{I} &= \mathbf{E} \mathbf{Y}_T = (200 \text{ V} \angle 0^\circ)(0.316 \text{ S} \angle -18.435^\circ) \\ &= \mathbf{63.2 \text{ A} \angle -18.44^\circ} \end{aligned}$$

b. Since the voltage is the same across parallel branches,

$$\mathbf{I}_1 = \frac{\mathbf{E}}{\mathbf{Z}_1} = \frac{200 \text{ V } \angle 0^\circ}{10 \, \Omega \angle 0^\circ} = \mathbf{20 \text{ A } \angle 0^\circ}$$

$$\mathbf{I}_2 = \frac{\mathbf{E}}{\mathbf{Z}_2} = \frac{200 \text{ V } \angle 0^\circ}{5 \, \Omega \angle 53.13^\circ} = \mathbf{40 \text{ A } \angle -53.13^\circ}$$

$$\mathbf{I}_3 = \frac{\mathbf{E}}{\mathbf{Z}_3} = \frac{200 \text{ V } \angle 0^\circ}{10 \, \Omega \angle -36.87^\circ} = \mathbf{20 \text{ A } \angle +36.87^\circ}$$

c. $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3$

$$\begin{aligned} 60 - j 20 &= 20 \angle 0^\circ + 40 \angle -53.13^\circ + 20 \angle +36.87^\circ \\ &= (20 + j 0) + (24 - j 32) + (16 + j 12) \end{aligned}$$

$$60 - j 20 = 60 - j 20 \quad (\text{checks})$$

d. $\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.316 \text{ S } \angle -18.435^\circ}$
 $= \mathbf{3.17 \, \Omega \angle 18.44^\circ}$



Thank You

