

Introduction to Electrical Circuits

Final Term Lecture - 05

Reference Book:

Introductory Circuit Analysis

Robert L. Boylestad, 11th Edition





W10	FC5	Chapter 18	18.2 SUPERPOSITION THEOREM	18.1, 18.2
			18.3 THÉVENIN'S THEOREM	18.8
	FC6	Chapter 18	18.4 NORTON'S THEOREM	18.15
			18.5 MAXIMUM POWER TRANSFER THEOREM	18.21



Superposition Theorem

The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.

- *Select a single source acting alone. Short the other voltage sources and open the current sources, if internal impedances are not known. If known, replace them by their internal impedances.*
- *Find the current through or the voltage across the required element, due to the source under consideration, using a suitable simplification technique.*
- *Repeat the above two steps for all the sources.*
- *Add all the individual effects produced by individual sources, to obtain the total current in or voltage across the element.*



EXAMPLE 18.1 Using the superposition theorem, find the current \mathbf{I} through the $4\ \Omega$ reactance (X_{L2}) in Fig. 18.1.

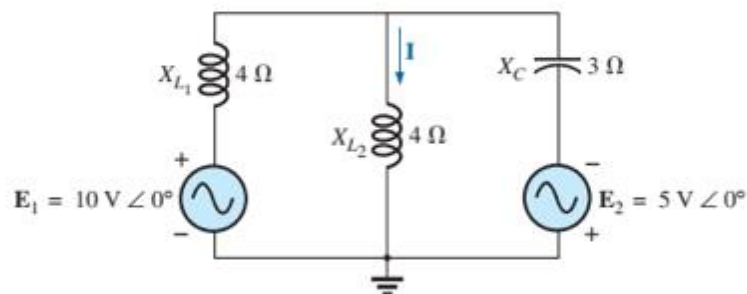


FIG. 18.1
Example 18.1.

Solution: For the redrawn circuit (Fig. 18.2),

$$\begin{aligned} \mathbf{Z}_1 &= +jX_{L1} = j4\ \Omega \\ \mathbf{Z}_2 &= +jX_{L2} = j4\ \Omega \\ \mathbf{Z}_3 &= -jX_C = -j3\ \Omega \end{aligned}$$

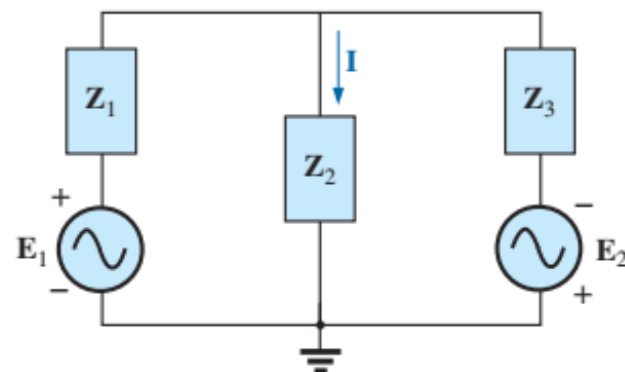


Fig. 18.2

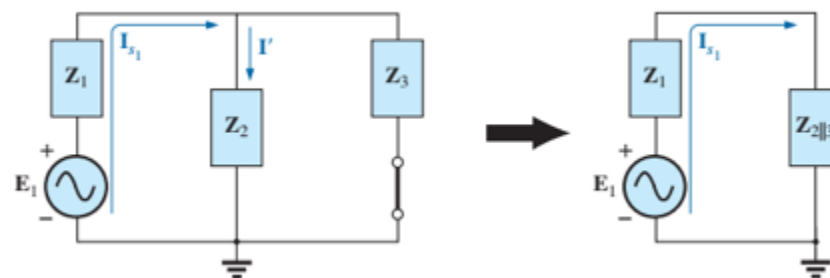


Fig. 18.3

Considering the effects of the voltage source \mathbf{E}_1 (Fig. 18.3), we have

$$\begin{aligned} \mathbf{Z}_{2||3} &= \frac{\mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_2 + \mathbf{Z}_3} = \frac{(j4\ \Omega)(-j3\ \Omega)}{j4\ \Omega - j3\ \Omega} = \frac{12\ \Omega}{j} = -j12\ \Omega \\ &= 12\ \Omega \angle -90^\circ \\ \mathbf{I}_{s1} &= \frac{\mathbf{E}_1}{\mathbf{Z}_{2||3} + \mathbf{Z}_1} = \frac{10\ \text{V} \angle 0^\circ}{-j12\ \Omega + j4\ \Omega} = \frac{10\ \text{V} \angle 0^\circ}{8\ \Omega \angle -90^\circ} \\ &= 1.25\ \text{A} \angle 90^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}' &= \frac{\mathbf{Z}_3 \mathbf{I}_{s1}}{\mathbf{Z}_2 + \mathbf{Z}_3} \quad (\text{current divider rule}) \\ &= \frac{(-j3\ \Omega)(j1.25\ \text{A})}{j4\ \Omega - j3\ \Omega} = \frac{3.75\ \text{A}}{j1} = 3.75\ \text{A} \angle -90^\circ \end{aligned}$$

Considering the effects of the voltage source E_2 (Fig. 18.4), we have

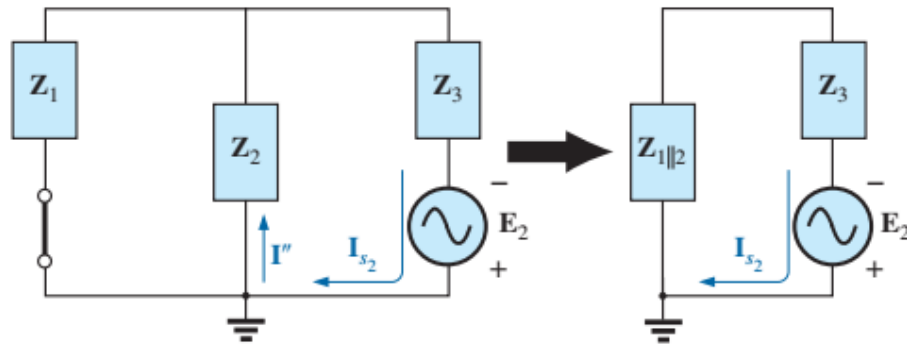


Fig. 18.4

$$Z_{1||2} = \frac{Z_1}{N} = \frac{j 4 \Omega}{2} = j 2 \Omega$$

$$I_{s2} = \frac{E_2}{Z_{1||2} + Z_3} = \frac{5 \text{ V } \angle 0^\circ}{j 2 \Omega - j 3 \Omega} = \frac{5 \text{ V } \angle 0^\circ}{1 \Omega \angle -90^\circ} = 5 \text{ A } \angle 90^\circ$$

and



$$I'' = \frac{I_{s2}}{2} = 2.5 \text{ A } \angle 90^\circ$$

The resultant current through the 4Ω reactance X_{L2} (Fig. 18.5) is

$$\begin{aligned} I &= I' - I'' \\ &= 3.75 \text{ A } \angle -90^\circ - 2.50 \text{ A } \angle 90^\circ = -j 3.75 \text{ A} - j 2.50 \text{ A} \\ &= -j 6.25 \text{ A} \\ I &= 6.25 \text{ A } \angle -90^\circ \end{aligned}$$

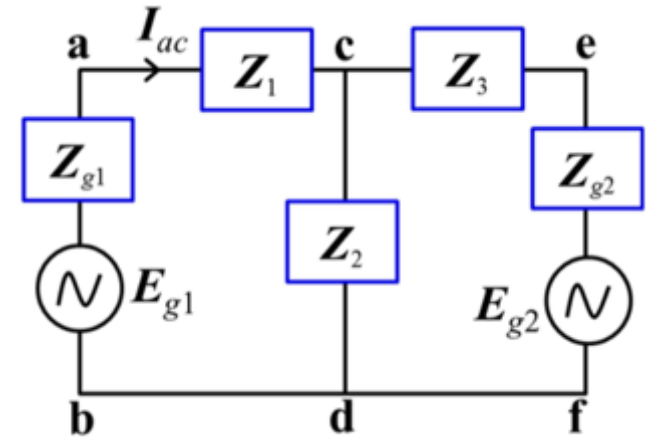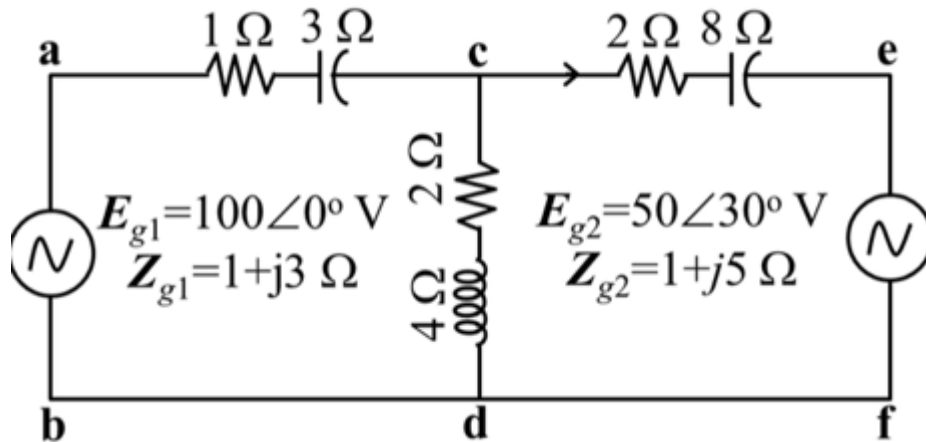Example

Calculate the current (using Superposition Theorem) in branch ac for the following network.



$$Z_1 = 1 - j3 \Omega$$

$$Z_2 = 2 + j4 \Omega$$




$$Z_3 = 2 - j8 \Omega$$

$$Z_{g1} = 1 + j3 \Omega$$

$$Z_{g2} = 1 + j5 \Omega$$



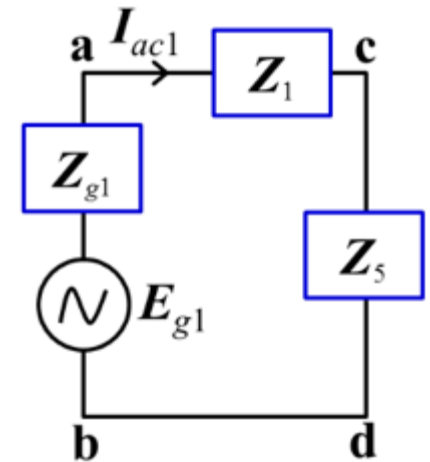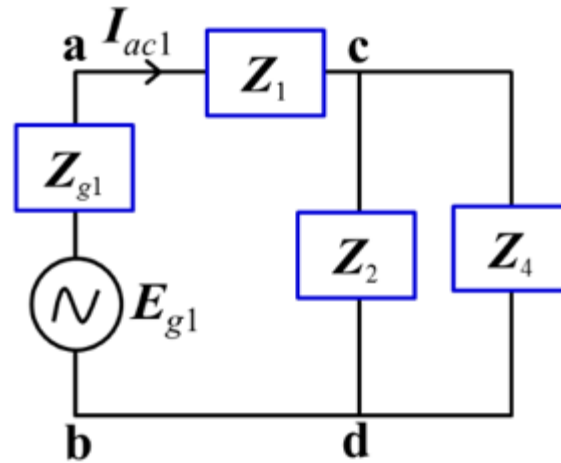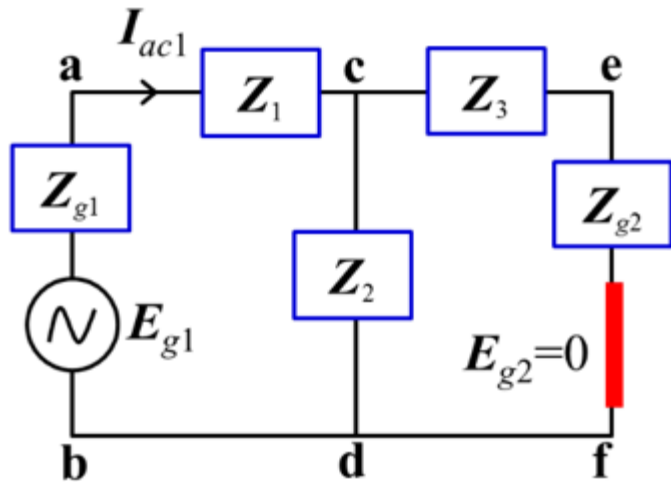Consider $E_{g1}=100\angle 0^\circ$ while set $E_{g1}=0$ i.e. short circuit.



$$Z_4 = Z_{g2} + Z_3 = 3 - j3 \Omega$$


$$Z_5 = \frac{Z_2 Z_4}{Z_2 + Z_4} = 3.7 + j0.46 \Omega$$

$$Z_{T1} = Z_{g1} + Z_1 + Z_5 = 5.7 + j0.46 \Omega$$

$$I_{ac1} = \frac{E_{g1}}{Z_{T1}} = 17.45 - j1.41 \text{ A}$$



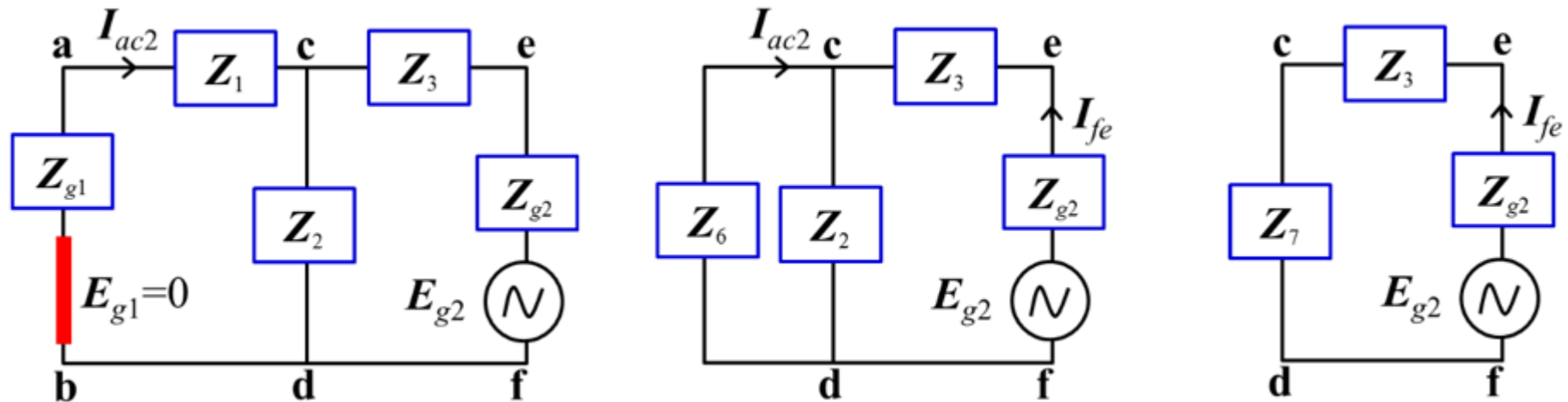Consider $E_{g2}=50\angle30^\circ$ while set $E_{g2}=0$ i.e. short circuit.



$$Z_6 = Z_{g1} + Z_1 = 2 \Omega \quad Z_7 = \frac{Z_2 Z_6}{Z_2 + Z_6} = 1.5 + j0.5 \Omega$$

$$Z_{T2} = Z_{g2} + Z_3 + Z_7 = 4.5 - j2.5 \Omega$$

$$I_{fe} = \frac{E_{g2}}{Z_{T2}} = 4.99 + j8.33 \text{ A}$$

$$I_{ac2} = -\frac{Z_2}{Z_2 + Z_6} I_{fe} = -1.66 - j7.5 \text{ A}$$

$$I_{ac} = I_{ac1} + I_{ac2} = 15.79 - j8.91 \text{ A}$$



EXAMPLE 18.2 Using superposition, find the current \mathbf{I} through the $6\ \Omega$ resistor in Fig. 18.6.

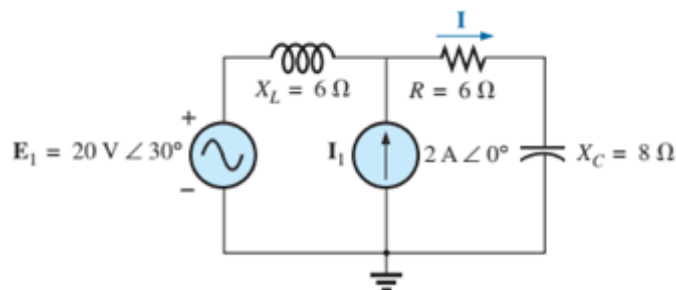


Fig. 18.6

Solution: For the redrawn circuit (Fig. 18.7),

$$\mathbf{Z}_1 = j6\ \Omega \quad \mathbf{Z}_2 = 6\ \Omega - j8\ \Omega$$

Consider the effects of the current source (Fig. 18.8). Applying the current divider rule, we have

$$\begin{aligned} \mathbf{I}' &= \frac{\mathbf{Z}_1 \mathbf{I}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(j6\ \Omega)(2\ \text{A})}{j6\ \Omega + 6\ \Omega - j8\ \Omega} = \frac{j12\ \text{A}}{6 - j2} \\ &= \frac{12\ \text{A} \angle 90^\circ}{6.32 \angle -18.43^\circ} \\ \mathbf{I}' &= 1.9\ \text{A} \angle 108.43^\circ \end{aligned}$$

Consider the effects of the voltage source (Fig. 18.9). Applying Ohm's law gives us

$$\begin{aligned} \mathbf{I}'' &= \frac{\mathbf{E}_1}{\mathbf{Z}_T} = \frac{\mathbf{E}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{20\ \text{V} \angle 30^\circ}{6.32\ \Omega \angle -18.43^\circ} \\ &= 3.16\ \text{A} \angle 48.43^\circ \end{aligned}$$

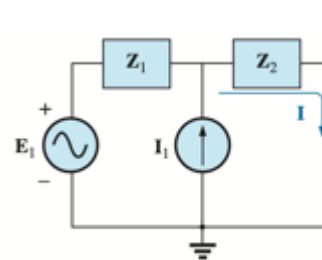


Fig. 18.7

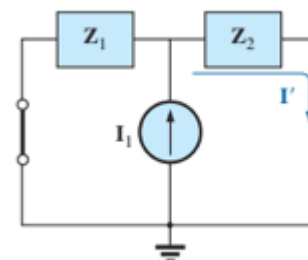


Fig. 18.8

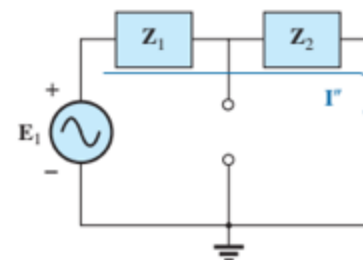



Fig. 18.9

The total current through the $6\ \Omega$ resistor (Fig. 18.10) is


$$\begin{aligned} \mathbf{I} &= \mathbf{I}' + \mathbf{I}'' \\ &= 1.9\ \text{A} \angle 108.43^\circ + 3.16\ \text{A} \angle 48.43^\circ \\ &= (-0.60\ \text{A} + j1.80\ \text{A}) + (2.10\ \text{A} + j2.36\ \text{A}) \\ &= 1.50\ \text{A} + j4.16\ \text{A} \\ \mathbf{I} &= 4.42\ \text{A} \angle 70.2^\circ \end{aligned}$$



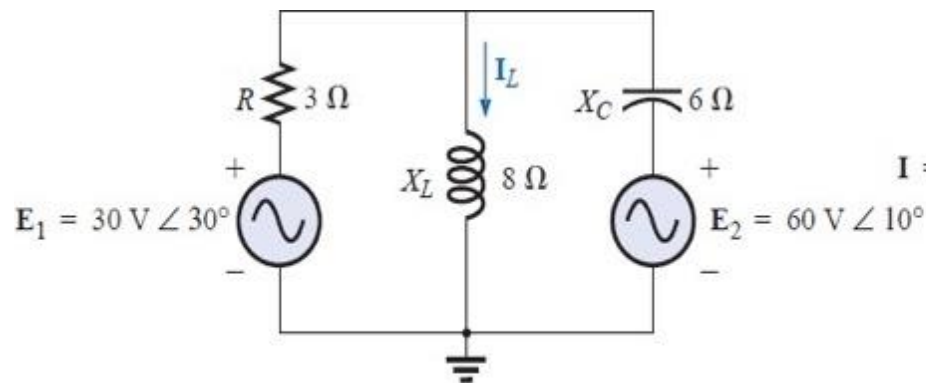
Problem: Using superposition, determine the current I_L for each network as shown in the following figure.




(a)

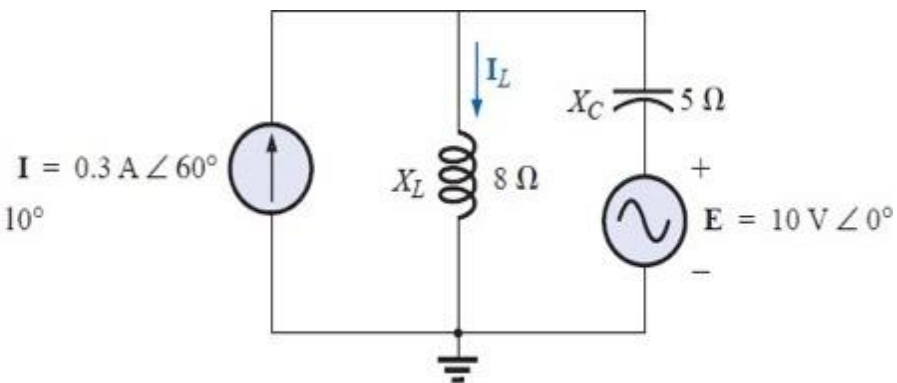

(b)

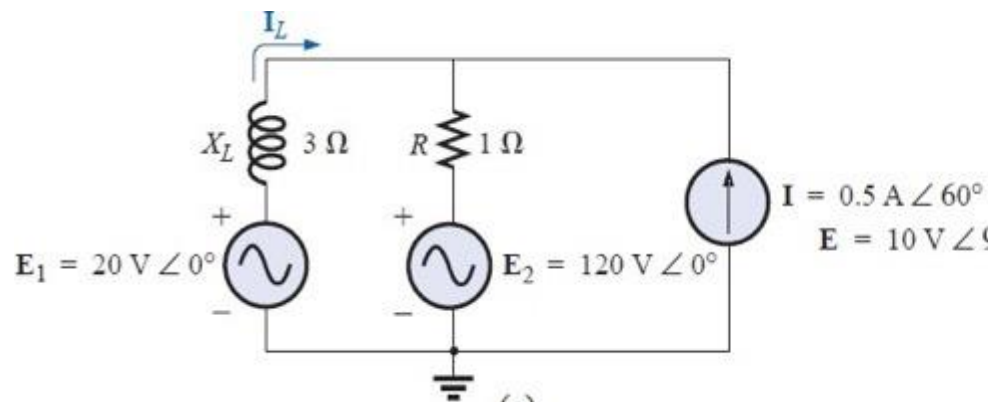

(c)

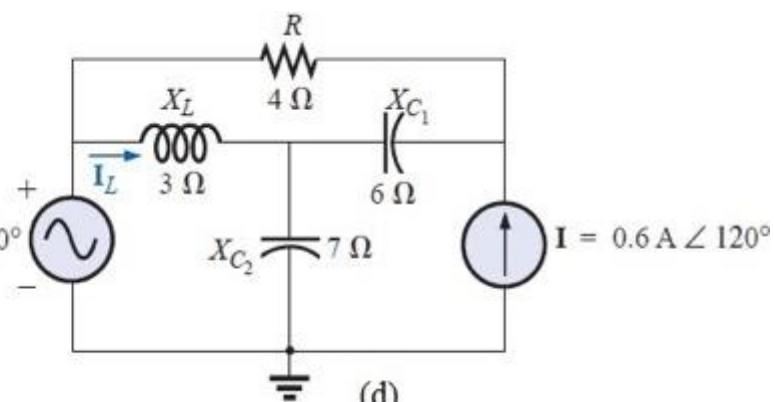



(d)

Thevenin's Theorem

Thévenin's theorem states the following:

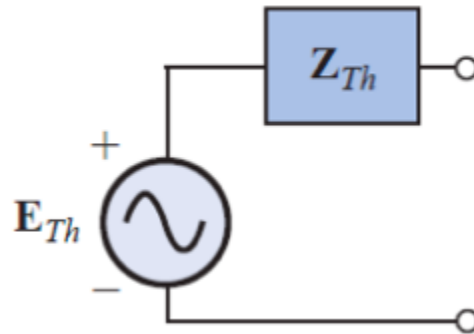
Any two-terminal, linear bilateral network can be replaced by an equivalent circuit consisting of a voltage source and a series impedance, as shown in the following figure.



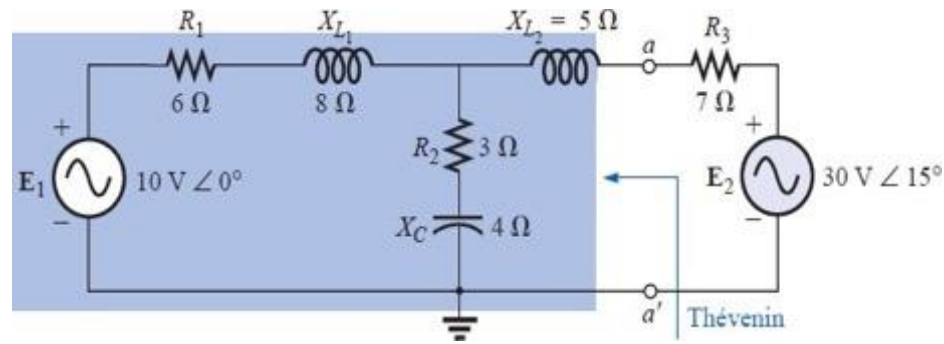


Calculate the Thevenin's Impedance (Z_{th}):

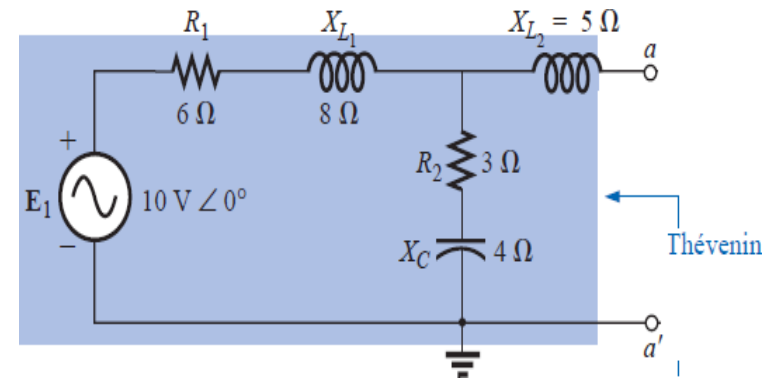Step 1: Remove that portion of the network across which the Thévenin equivalent circuit is to be found.



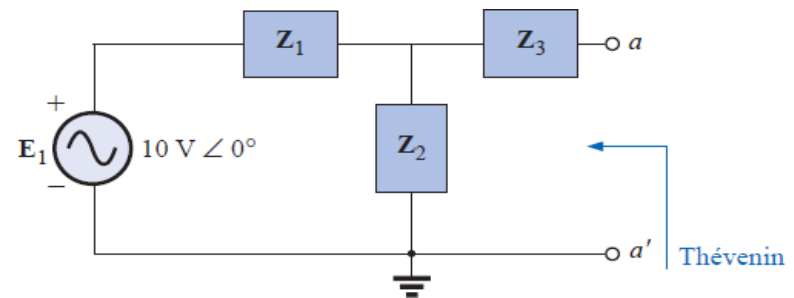Step 2: Mark the terminals of the remaining two-terminal network.




$$Z_1 = R_1 + jX_{L1} = 6 + j8 \, \Omega = 10 \angle 53.13^\circ \, \Omega$$

$$Z_2 = R_2 - jX_C = 3 - j4 \, \Omega = 5 \angle -53.13^\circ \, \Omega$$

$$Z_3 = jX_{L2} = j5 \, \Omega = 5 \angle 90^\circ \, \Omega$$

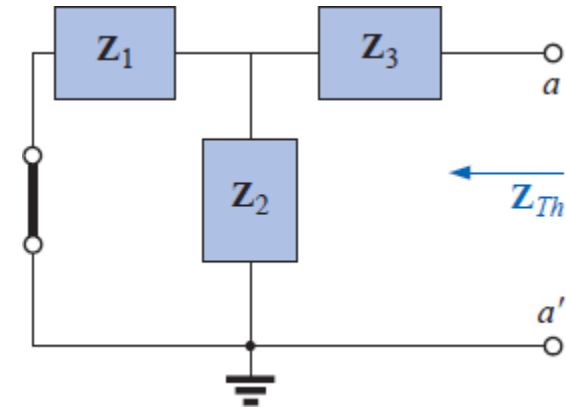Step 3: Set all sources to zero (**voltage sources are replaced by short circuits**, and **current sources by open circuits**). If the internal impedance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.



Step 4: Find the impedance between the two marked terminals.


$$\begin{aligned} Z_{Th} &= Z_3 + \frac{Z_1 Z_2}{Z_1 + Z_2} = j5 + \frac{(6 + j8)(3 - j4)}{6 + j8 + 3 - j4} \\ &= 4.64 + j2.94 \, \Omega = 5.49 \angle 32.36^\circ \end{aligned}$$



Calculate the Thevenin's Voltage (E_{th}):

Step 1: Remove that portion of the network across which the Thévenin equivalent circuit is to be found.

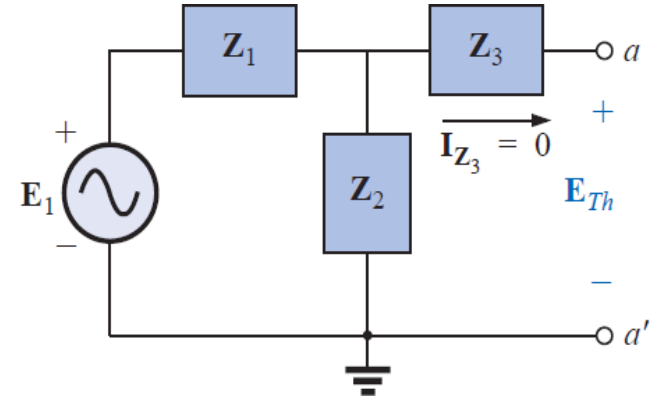
Step 2: Calculate the voltage drop across terminals of the remaining two-terminal network.




Since a - a' is an open circuit, $I_{Z_3} = 0$. Then E_{Th} is the voltage drop across Z_2 :
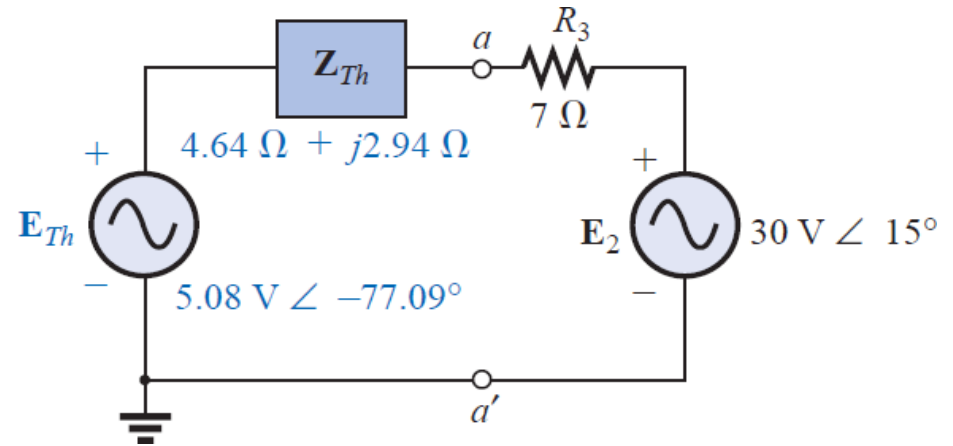
$$\begin{aligned} E_{Th} &= \frac{Z_2 E}{Z_1 + Z_2} (\text{VDR}) = \frac{(3 - j4)(10 + j0)}{6 + j8 + 3 - j4} \\ &= 5.08 \angle -77.09^\circ \end{aligned}$$






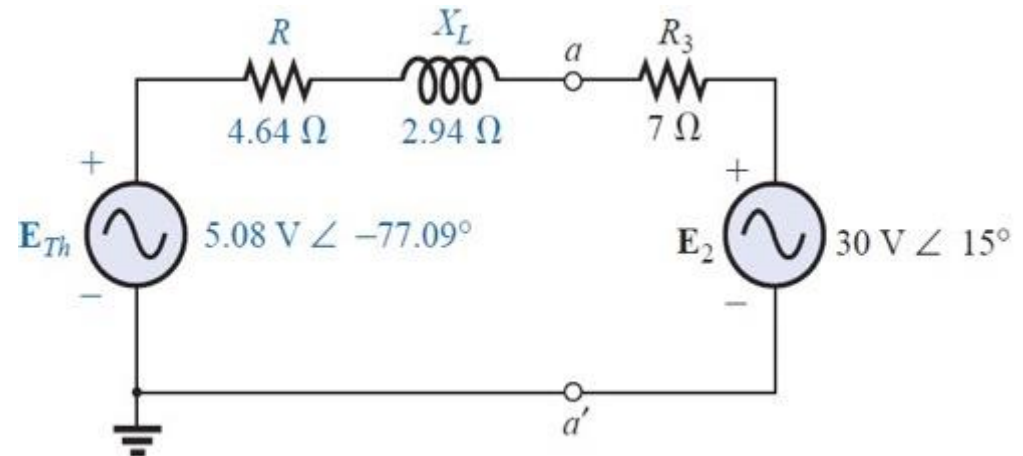Finally draw the Thevenin's equivalent circuit by connecting the removed part.




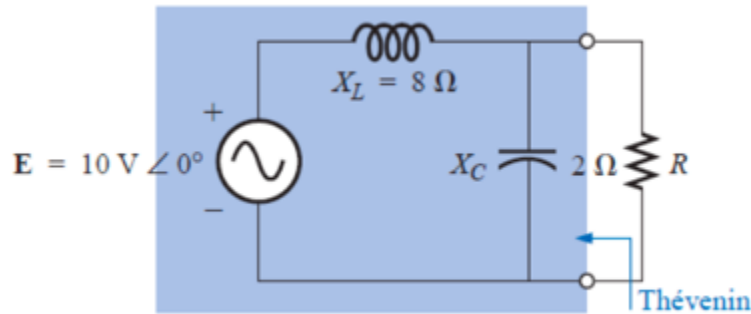
Example

Determine the Thevenin equivalent circuit for the network external to the R resistor of following figure.




$$Z_1 = j8\ \Omega$$

$$Z_2 = -j2\ \Omega$$

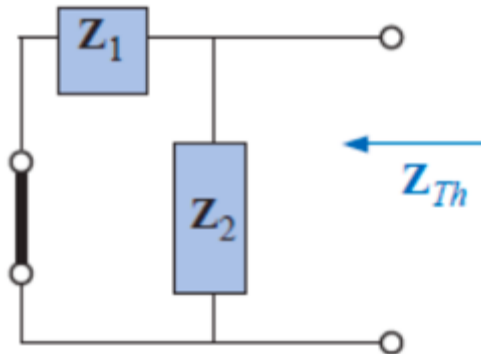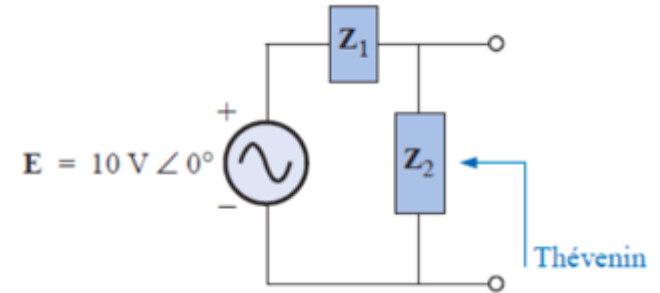

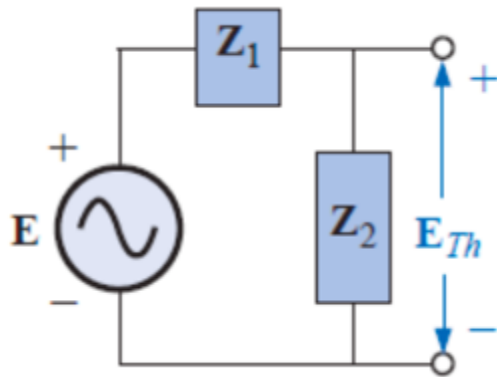
$$Z_{Th} = \frac{Z_1 Z_2}{Z_1 + Z_2} = 2.67 \angle -90^\circ$$






$$E_{Th} = \frac{Z_2 E}{Z_1 + Z_2} (\text{VDR}) = 3.33 \angle -180^\circ$$



Thevenin equivalent circuit shown in the following figure.

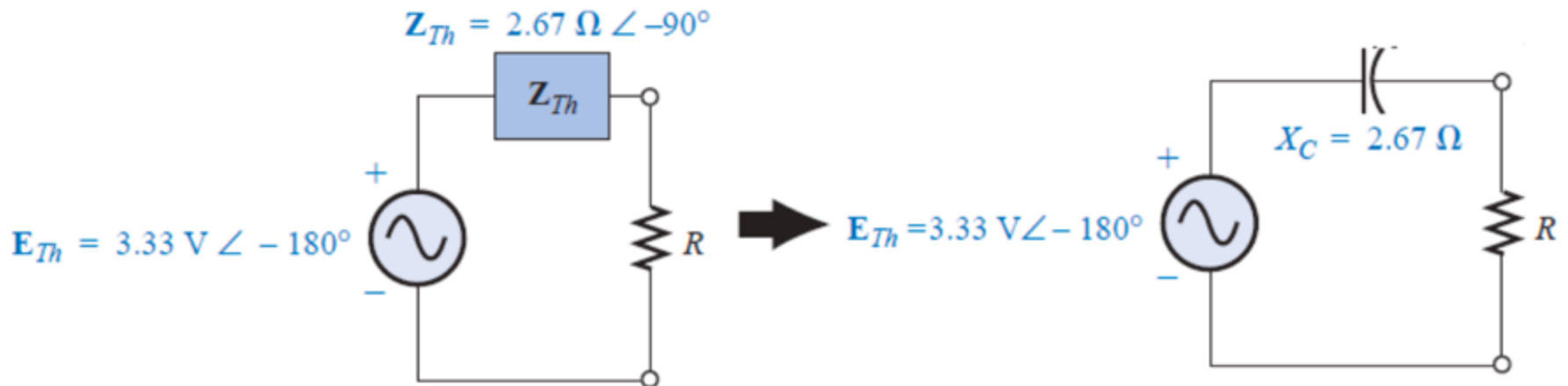

Problem 1: Find the Thévenin equivalent circuit for the portions of the networks of following figures external to the elements between points a and b.

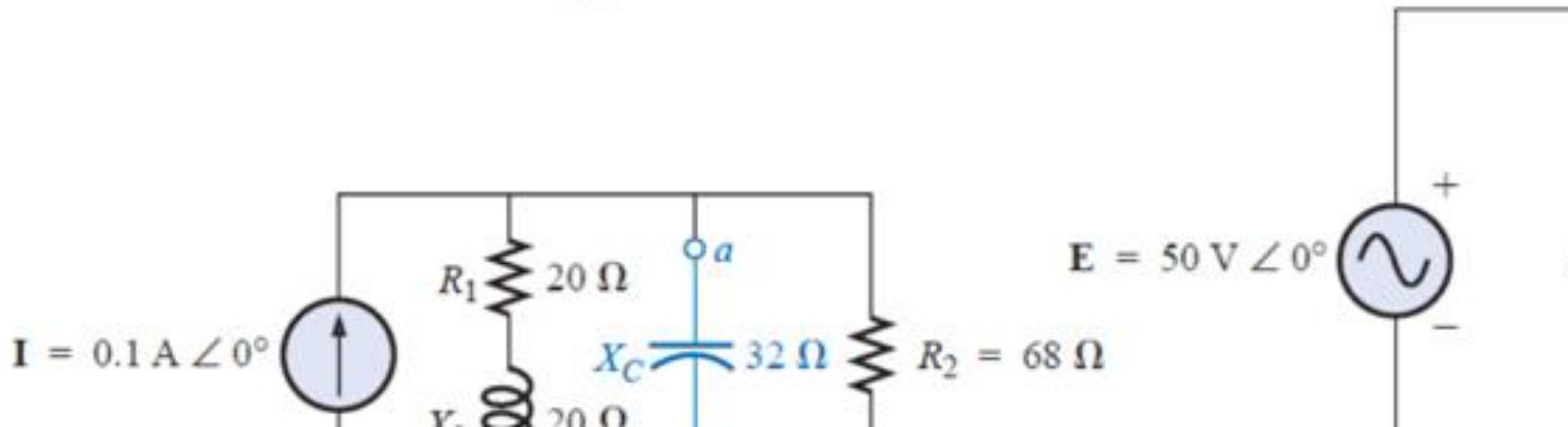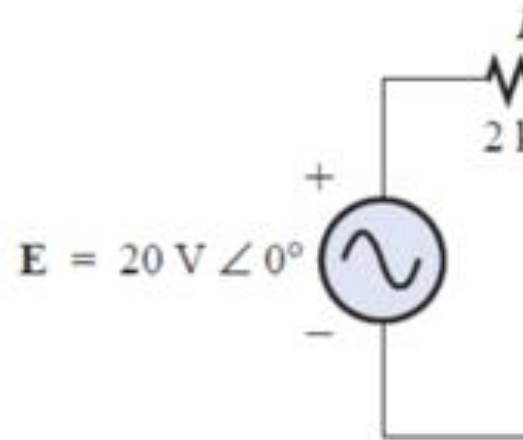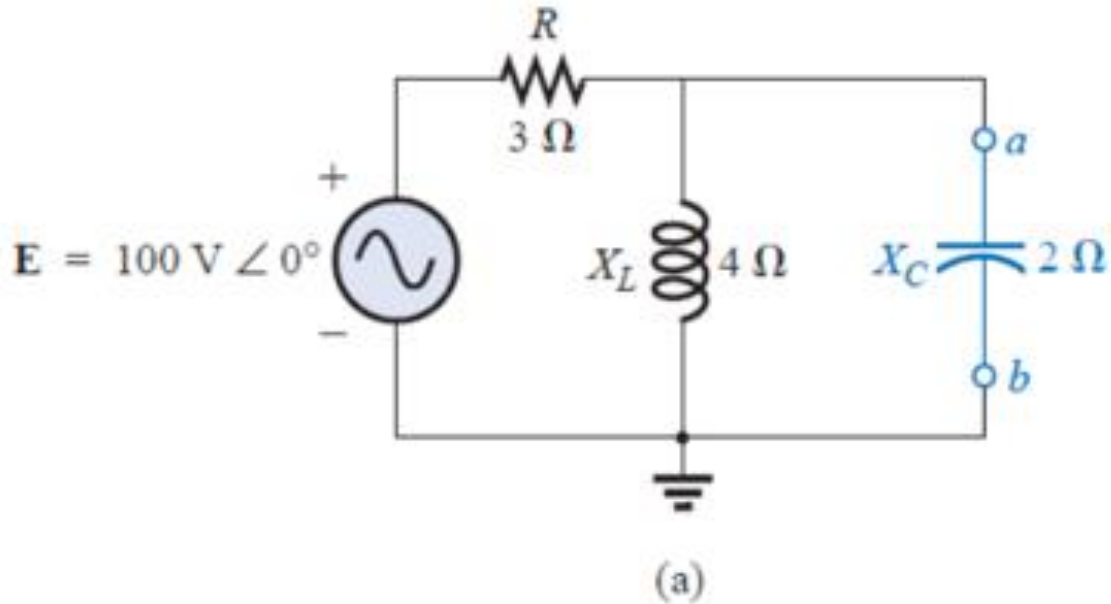

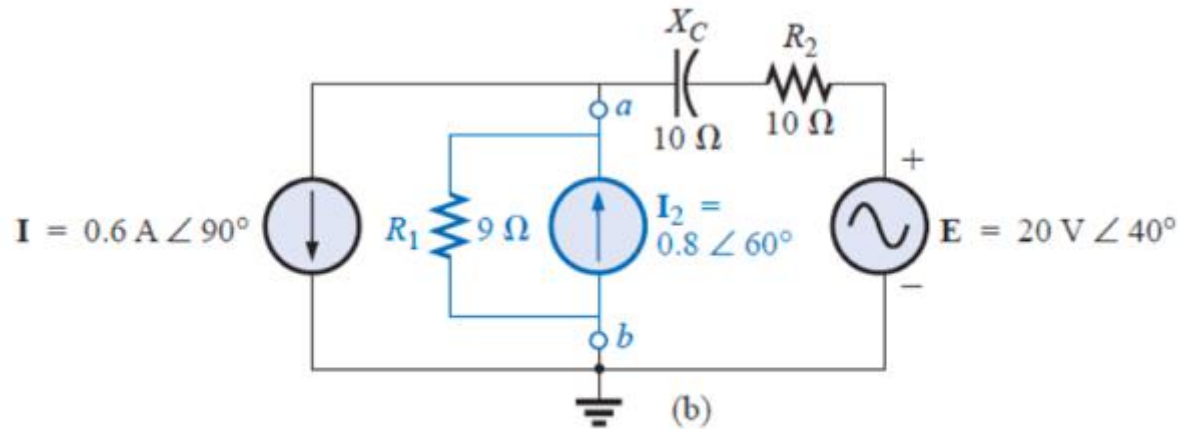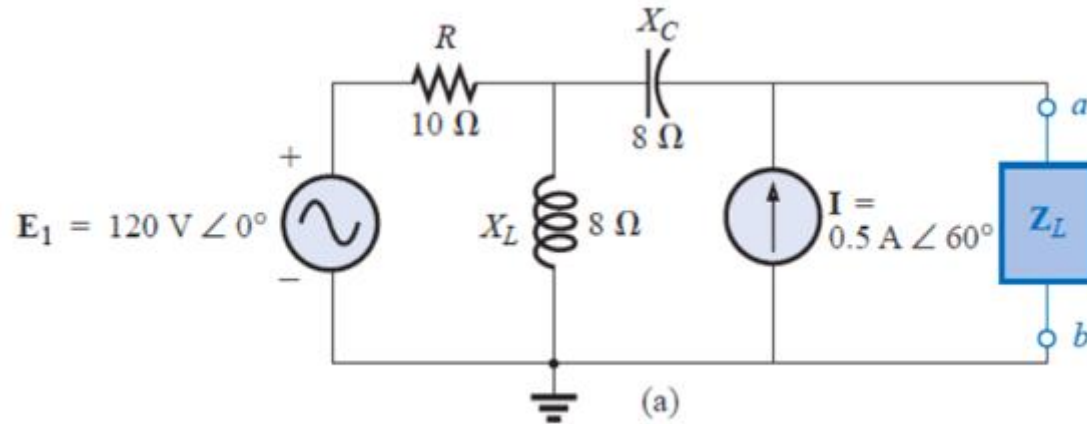Problem 2: Find the Thévenin equivalent circuit for the portions of the networks of following figures external to the elements between points a and b.



Thank You

