



American International University- Bangladesh (AIUB)

Faculty of Engineering (EEE)

Course Name:	Introduction to Electrical Circuits (IEC) Lab	Course Code:	EEE 2109
Semester:	Summer 2021-22	Sec:	W
Faculty:	DR.MD.KABIRUZZAMAN		

Task:	Perform Open End Lab following given instructions.
Experiment title:	Analysis of RLC parallel circuit and verification of KCL in AC circuits.

Student Name:	Pranto Biswas	Student ID:	21-45026-2
----------------------	---------------	--------------------	------------

Group Members	ID	Name
1.	21-44989-2	SK MUKTADIR HOSSAIN
2.	21-45026-2	PRANTO BISWAS
3.	22-46386-1	KAZI ABDULLAH JARIF
4.	22-46313-1	MD. NESAR UDDIN

CO1: Function as effective team leader/member in multi-disciplinary problems

Marking Rubrics (to be filled by Faculty)

	Objectives	Unsatisfactory (0-1)	Good (2-3)	Excellent (4-5)	Marks
Performance (20)	Identify experiment goals	Cannot identify goals	Can identify some goals but unable to draw adequate hypothesis	Can identify necessary and sufficient goals	
	Setup of experiment	Cannot setup experiment without support	Can setup some of the portions of experiment without support	Can setup the whole experiment without support	
	Take organized and accurate measurement	Cannot take measurements	Can take measurements but inaccurately	Can take organized and accurate measurements	
	Summarize findings and compare actual to expected results	Cannot summarize or compare findings to expected results	Summarize finding in an incomplete way	Summarize finding in a complete way	
Viva (10)	Viva Observation 1	Cannot answer any question related to the experimental setup	Can answer some of the questions	Can answer most or all the questions	
	Viva Observation 2	Unexpected experimental outcome between calculated data and experimented data	Somewhat unexpected experiment outcome	Accurate data collected from the hardware	
	Comments	Assessed by (Name, Sign, and Date)	Total (out of 30):		

Table of contents

Topics	Page no.
Title Page	1
Table of Content	2
1.Objective	3
2. Equipment	3-4
3. Procedure	5-11
4. Result and Data analysis	12-14
5. Conclusion	14

1.Objectives:

The RC & RL circuit is used to determine the input and output relationship of voltage and current for different frequencies. In RC series circuit the voltage lags the current by 90° and in RL series circuit the voltage leads the current by 90° .



An RLC circuit is an electrical circuit consisting of a resistor, an inductor, and a capacitor, connected in series. The RLC part of the name is due to those letters being the usual electrical symbols for resistance, inductance, and capacitance respectively. Series RLC circuits are classed as second-order circuits because they contain two energy storage elements, an inductance and a capacitance

The primary objectives of the lab experiment are-

- To determine the reactance of the RL and RC circuits and the impedance equation both practically and theoretically.
- To determine phase relationship between voltage and current in an RLC circuit.
- To draw the complete vector diagram.
- Design an RLC series circuit and verify KVL.

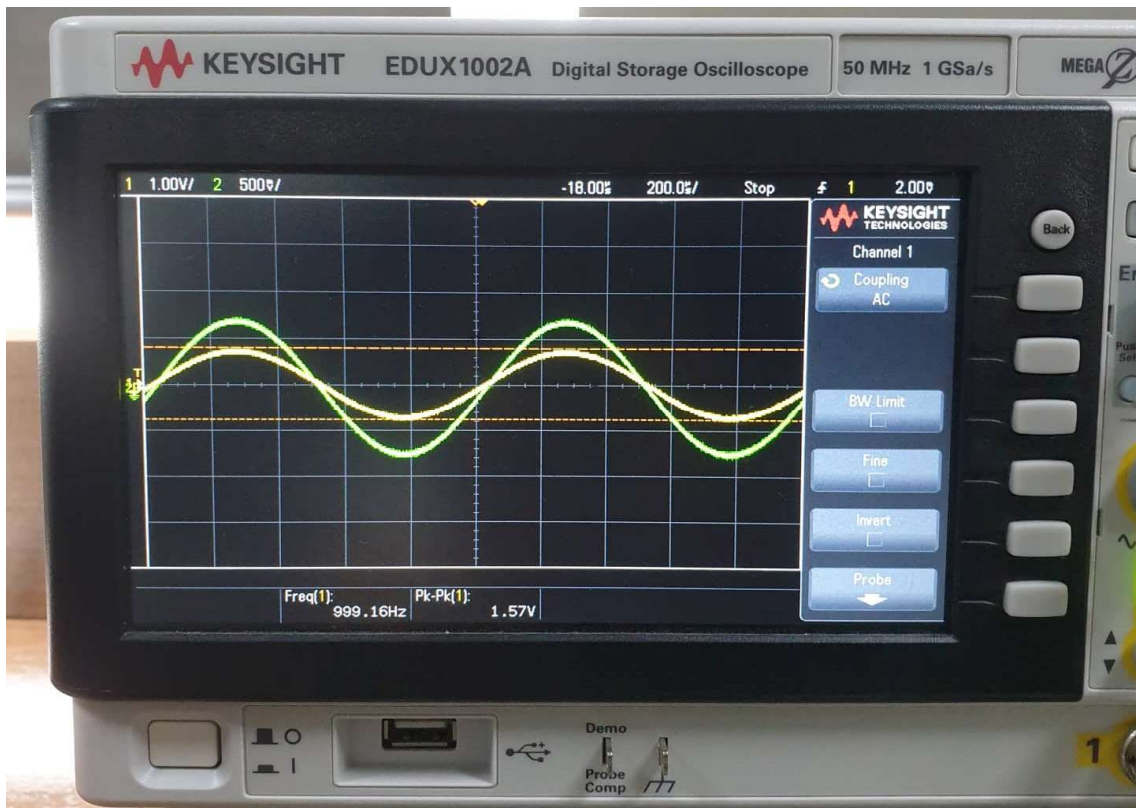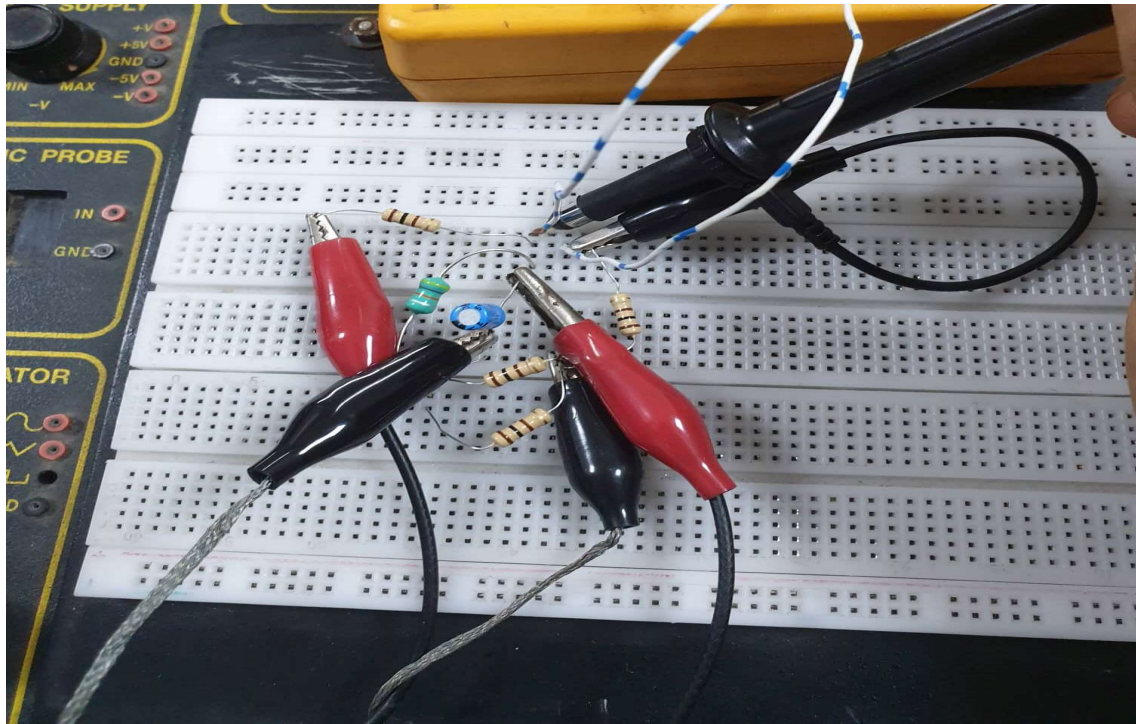2.Equipment:

- Oscilloscope
- Function generator
- Resistor: $98\ \Omega$ (3)
- Inductor: 10 mH
- Capacitor: $1\ \mu\text{F}$
- Connecting wire.
- Bread board



3.Procedure:

In DC circuits, conductance (G) was defined as being equal to $1/R$. The total conductance of a parallel circuit was then found by adding the conductance of each branch. The total resistance R_T is simply $1/G_T$. In ac circuits, we define admittance (Y) as being equal to $1/Z$. The unit of measure for admittance as defined by the *SI* system is Siemens, which has the symbol S.

Admittance is a measure of how well an ac circuit will admit, or allow, current to flow in the circuit. The larger its value, therefore, the heavier the current flow for the same applied potential. The total admittance of a circuit can also be found by finding the sum of the parallel admittances.

The total impedance Z_T of the circuit is then $1/Y_T$ that is, for the network of Fig.1

$$Y_T = Y_1 + Y_2 + Y_3 + \dots + Y_N$$

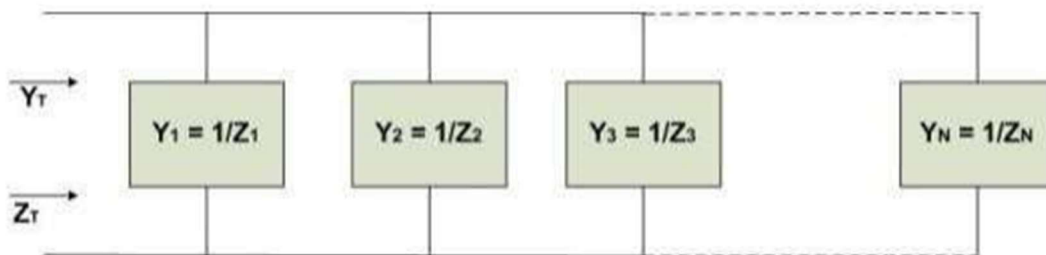


Fig.1: Parallel Branch Equivalent Admittance

Or, Since $Z = 1/Y$,

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

For two impedances in parallel,

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

For three parallel impedances,

$$Z_T = \frac{Z_1 Z_2 Z_3}{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}$$

As pointed out in the introduction to this section, conductance is the reciprocal of resistance

$$Y_R = \frac{1}{Z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$

The reciprocal of reactance ($1/X$) is called susceptance and is a measure of how susceptible an element is to the passage of current through it. Susceptance is also measured in Siemens and is represented by the capital letter B.

For the inductor,

$$Y_L = \frac{1}{Z_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ$$

Defining

$$B_L = \frac{1}{X_L} \text{ (siemens, S)}$$

$$Y_L = B_L \angle -90^\circ$$

For inductance, an increase in frequency or inductance will result in a decrease in susceptance or, correspondingly, in admittance.

For the capacitor,

$$Y_C = \frac{1}{Z_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ$$

Defining

$$B_C = \frac{1}{X_C} \text{ (siemens, S)}$$

$$Y_C = B_C \angle 90^\circ$$

For the capacitor, therefore, an increase in frequency or capacitance will result in an increase in its susceptibility.

For any configuration (series, parallel, series-parallel, etc.), the angle associated with the total admittance is the angle by which the source current leads the applied voltage. For inductive networks, θT is negative, whereas for capacitive networks, θT is positive.

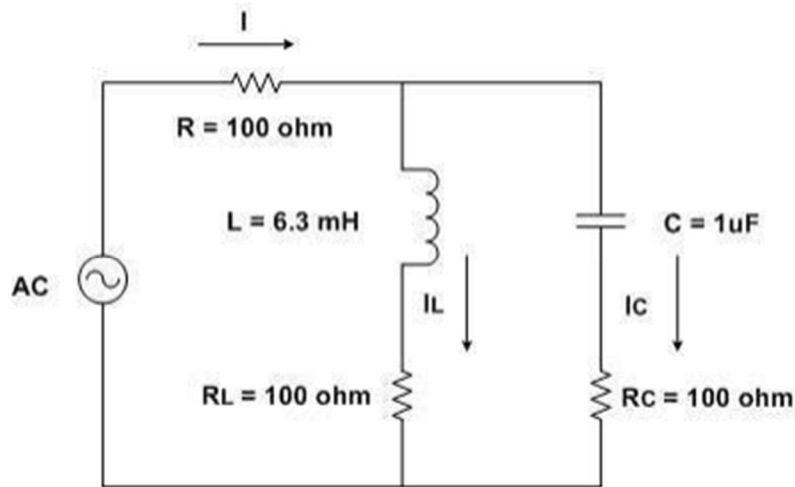


Fig. 2: Parallel Circuit KCL verification

The circuit of fig.2 represents a RLC parallel circuit where the Total Current I will divide into IL and IC in the parallel branches. If we apply KCL, $I = IL + IC$.

Experimental Procedure


1. We constructed the circuit as shown in fig.1. connected channel 1 of the oscilloscope across function generator and channel 2 of the oscilloscope across RL
2. Then we have set the amplitude of the input signal 5V peak and the frequency at 1 kHz and selected sinusoidal wave shape.
3. We measured the value of V_{RL} and I_L
4. Then we determined phase relationship between E and V_{RL} (i.e., θ_L)
5. Connected channel 2 of oscilloscope across RC .
6. Determined phase relationship between the waves.
7. Measured value of V_{RC} and I_C .
8. Determined phase relationship between E and V_{RC} (i.e., θ_C)
9. Added I_L and I_C .
10. Measured V_R and I connecting channel 2 across R .
11. Compared $I_L + I_C$ with the practically obtained value of I .
12. Did the same work for setting input frequency 2 kHz


Data Table

Freq.(f) (kHz)	I (A)	θ (°)	I_R (A)	θ_R (°)	I_L (A)	θ_L (°)	I_C (A)	θ_C (°)
1	$0.0089 + j0.0000106$	$0.0089 \angle 0.683^\circ$	0.0089	$\angle 0.0683^\circ$	0.0075	$\angle -32.62^\circ$	0.0048	$\angle 57.29^\circ$
2	$0.00893 + j0.0000723$	$0.00893 \angle 0.46^\circ$	0.00893	$\angle 0.046^\circ$	0.0055	$\angle -51.98^\circ$	0.0071	$\angle 37.9^\circ$


Simulation


For 1 kHz

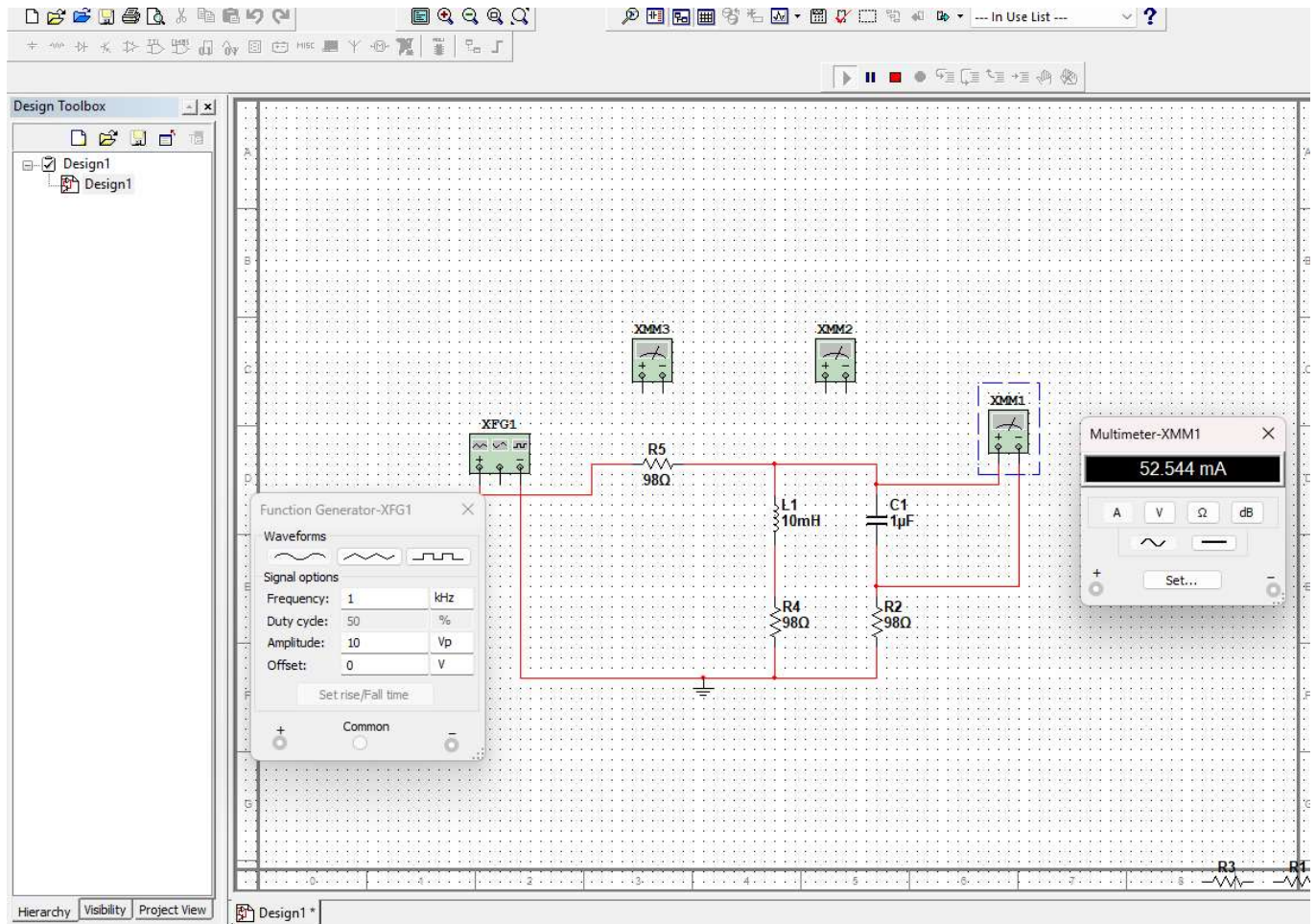

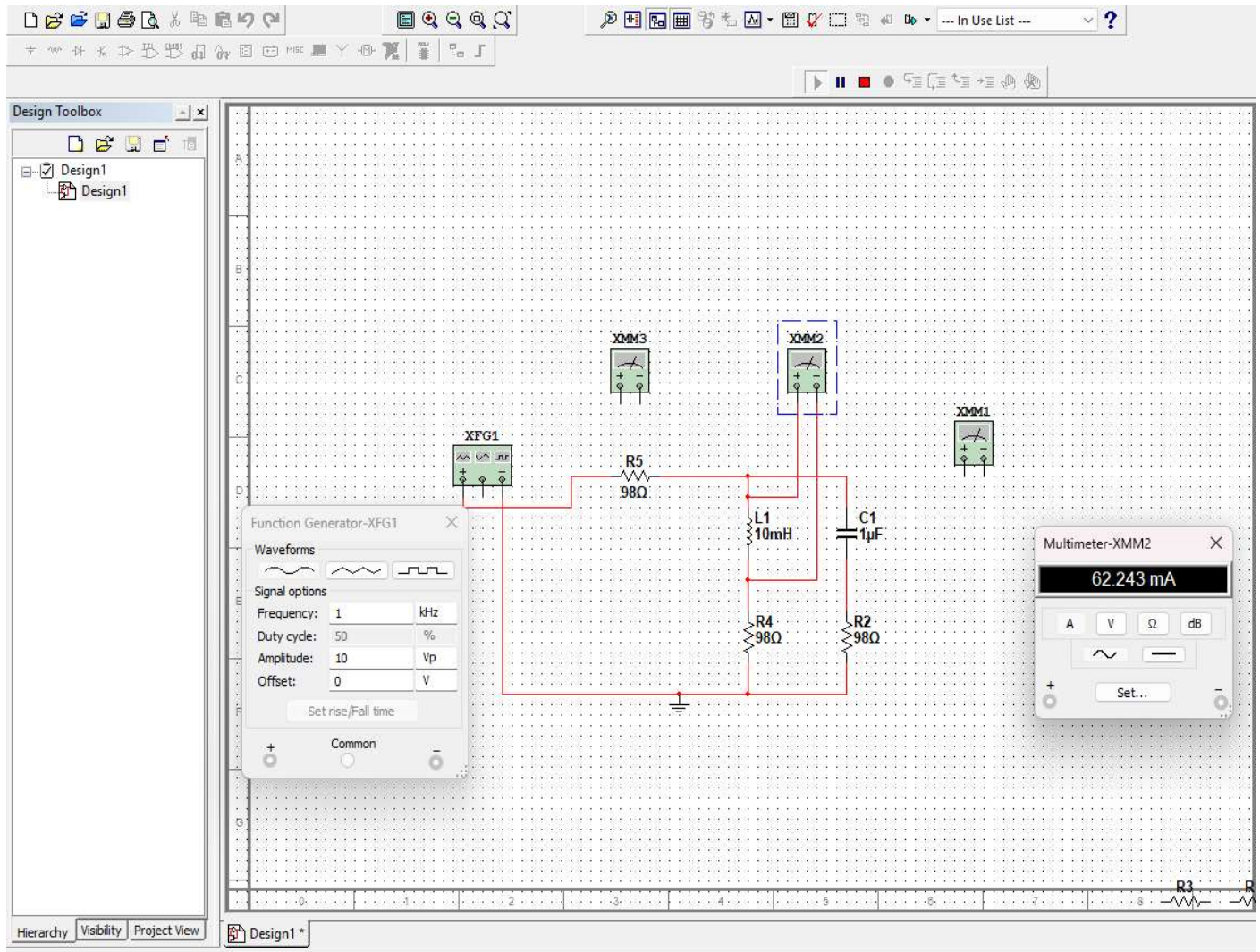


For 2 kHz

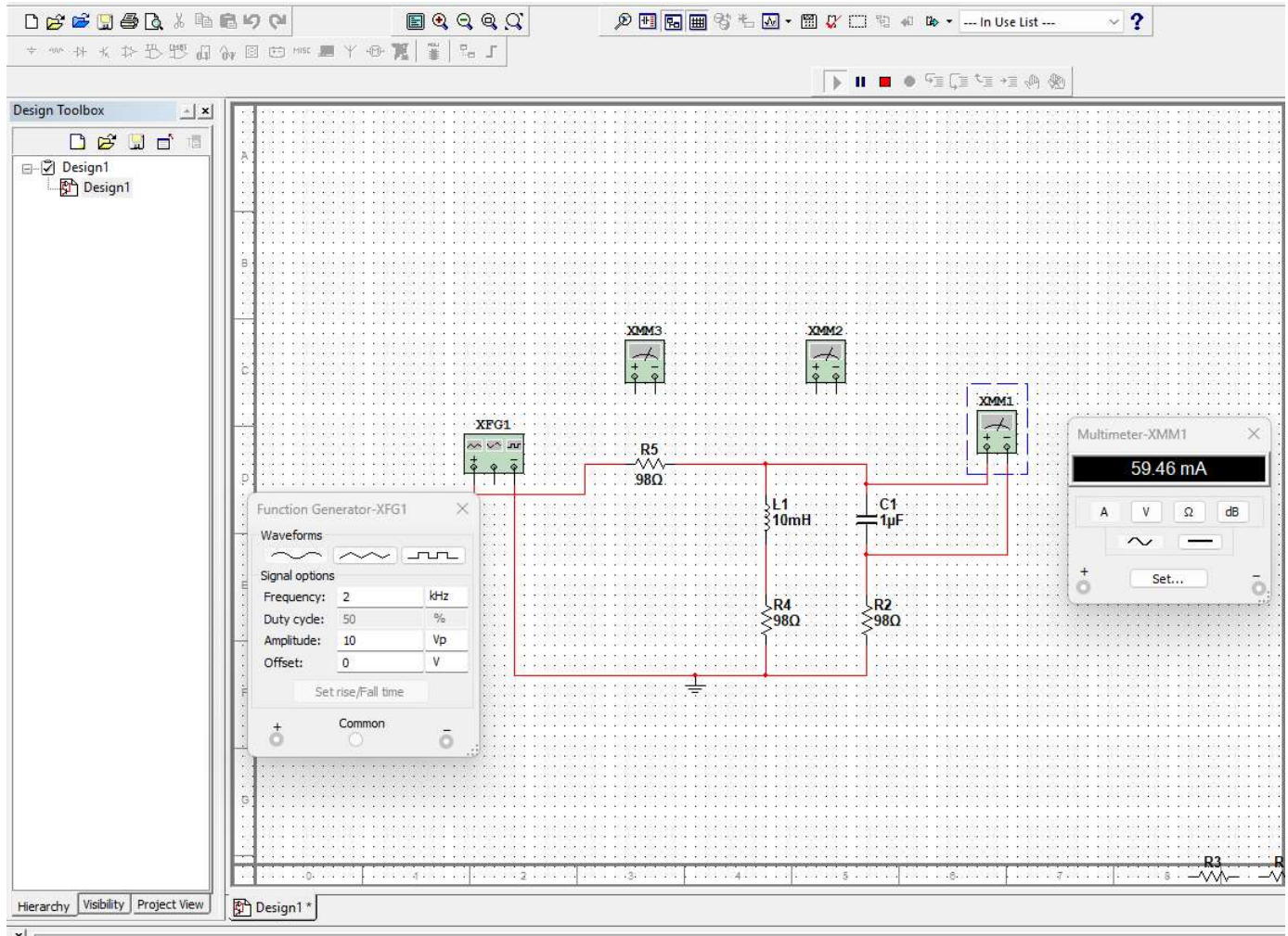

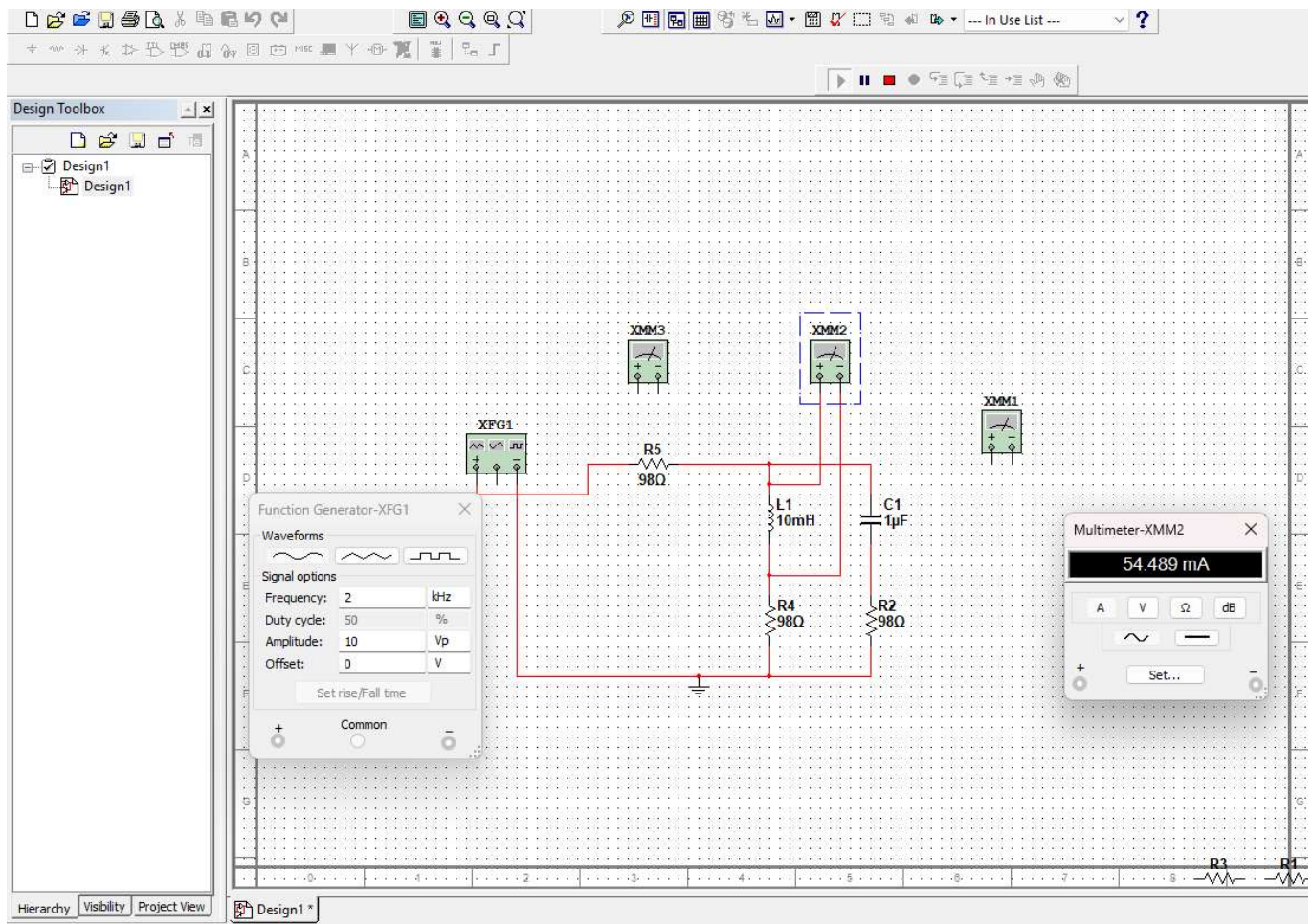

4. Results and Data analysis:

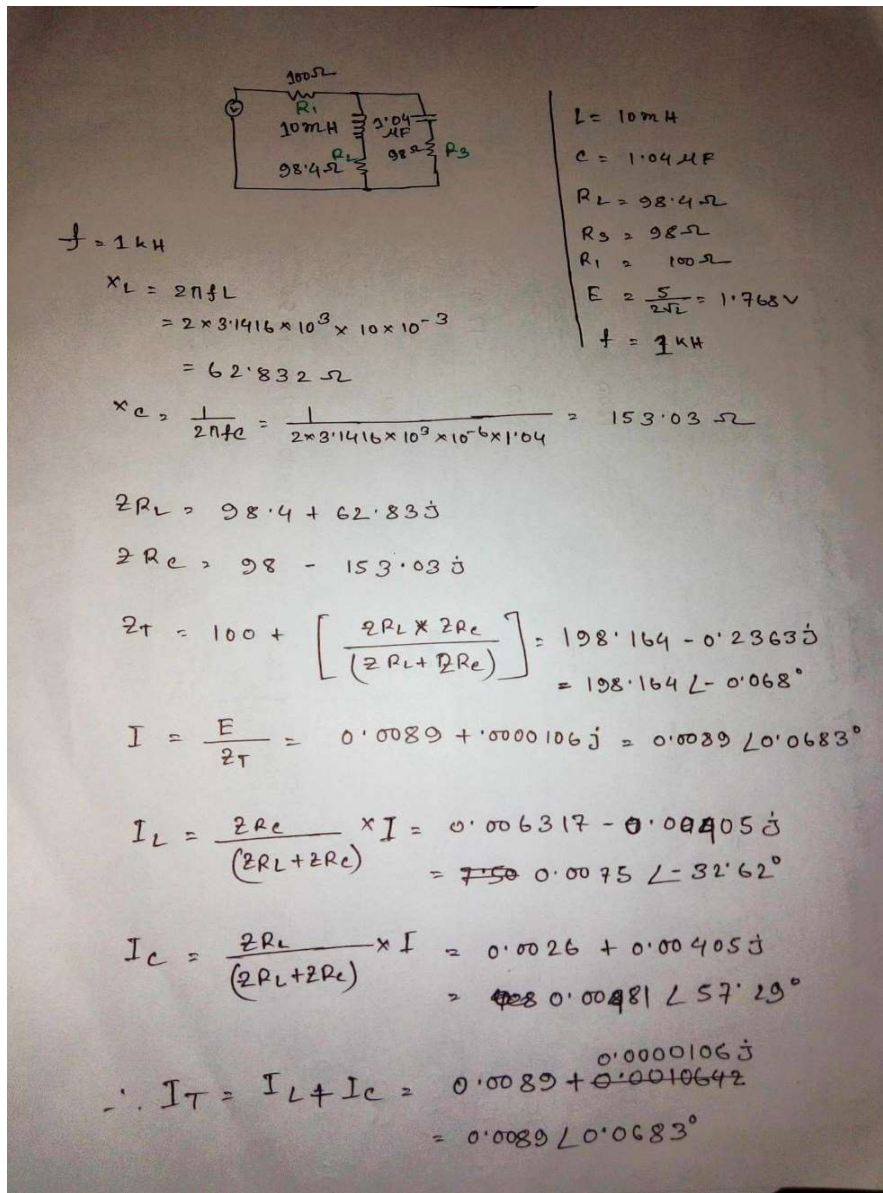

The image shows a handwritten circuit diagram and a series of calculations for an AC circuit. The circuit diagram at the top left shows a voltage source E connected in series with a resistor R_1 (100 Ω). This is followed by a parallel combination of an inductor branch (with inductor L and resistor R_L in series) and a capacitor branch (with capacitor C and resistor R_C in series). The total current is I , the current through the inductor branch is I_L , and the current through the capacitor branch is I_C .

Given values and calculations:

- $f = 1 \text{ kHz}$
- $X_L = 2\pi fL = 2 \times 3.1416 \times 10^3 \times 10 \times 10^{-3} = 62.832 \Omega$
- $X_C = \frac{1}{2\pi fC} = \frac{1}{2 \times 3.1416 \times 10^3 \times 10^{-6} \times 1.04} = 153.03 \Omega$
- $Z_{RL} = 98.4 + j62.833$
- $Z_{RC} = 98 - j153.03$
- $Z_T = 100 + \left[\frac{Z_{RL} \times Z_{RC}}{Z_{RL} + Z_{RC}} \right] = 198.164 - j0.23633 = 198.164 \angle -0.068^\circ$
- $I = \frac{E}{Z_T} = \frac{1.768 \text{ V}}{198.164 \angle -0.068^\circ} = 0.0089 + j0.000106 = 0.0089 \angle 0.0683^\circ$
- $I_L = \frac{Z_{RC}}{Z_{RL} + Z_{RC}} \times I = \frac{98 - j153.03}{98.4 + j62.833 + 98 - j153.03} \times I = 0.006317 - j0.004405 = 0.0075 \angle -32.62^\circ$
- $I_C = \frac{Z_{RL}}{Z_{RL} + Z_{RC}} \times I = \frac{98.4 + j62.833}{98.4 + j62.833 + 98 - j153.03} \times I = 0.0026 + j0.00405 = 0.00481 \angle 57.29^\circ$
- $\therefore I_T = I_L + I_C = 0.0089 + j0.000106 = 0.0089 \angle 0.0683^\circ$

$$\begin{aligned}
 f &= 2 \text{ kHz} \\
 E &= \frac{5}{2\sqrt{2}} = 1.768 \text{ V} \\
 X_L &= 2\pi f L = 125.663 \Omega \\
 X_C &= \frac{1}{2\pi f C} = 76.517 \Omega \\
 Z_{RL} &= 98.4 + j125.663 \\
 Z_{RC} &= 98.4 - j76.517 \\
 Z_T &= R_1 + \left(\frac{Z_{RL} \times Z_{RC}}{Z_{RL} + Z_{RC}} \right) = 198.017 - j0.16 \Omega \\
 I &= \frac{E}{Z_T} = 0.00893 + j0.00000721 \text{ A} \\
 &= 0.00893 \angle 0.046^\circ \\
 I_L &= \frac{Z_{RC}}{Z_{RL} + Z_{RC}} \times I = 0.00337 - j0.0043 \text{ A} \\
 &= 0.0055 \angle -51.92^\circ \\
 I_C &= \frac{Z_{RL}}{Z_{RL} + Z_{RC}} \times I = 7.034 \times 10^{-3} + j0.0043 \text{ A} \\
 &= 0.0071 \angle 37.9^\circ \\
 I_T &= 0.00893 + j0.00000723 \text{ A} = 0.00893 \angle 0.046^\circ
 \end{aligned}$$

From simulation for 1 kHz

$$I_C = 0.0052 \quad \text{and} \quad I_L = 0.0062$$

From calculation for 1kHz

$$I_C = 0.0048 \quad \text{and} \quad I_L = 0.0075$$

From simulation for 2 kHz

$$I_c = 0.00595 \quad \text{and} \quad I_L = 0.00544$$

From calculation for 2kHz

$$I_c = 0.0071 \quad \text{and} \quad I_L = 0.0055$$

5.Conclusion

- ✓ In this experiment, RC, RL, RLC series circuits were constructed.
- ✓ Input shape, frequency, wave shape was modified as required. I , V_R , V_L & V_C were measured where necessary.
- ✓ The frequency input signal's value was adjusted several times. The obtained data was inserted into the table.
- ✓ The values obtained from simulation and calculation are almost similar.
- ✓ Relevant calculation was done using the experimental data. The analysis and verification were completed effectively.

If we apply KCL, $I = I_L + I_C$